Temperature Sensor and the Serial Monitor

This simple project will take a temperature reading from the Temp Sensor and relay the findings to the Serial Monitor.

To build our circuit with Arduino Uno, follow the steps below:

- Connect Arduino Uno GND to LM35 GND
- 2. Connect Arduino 5V pin to LM35 pin 1
- 3. Connect Arduino Uno Analog Pin 1 to LM35 pin OUT

Arduino code below(calculates for Celsius)

